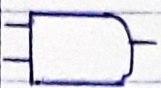
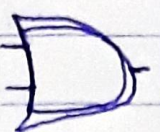
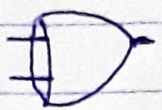
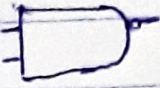
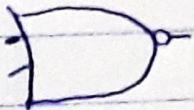


Practical 5

Part A 1. Logic gates

Inputs outputs truth table

A	B	AND	OR	XOR	NAND	NOR
0	0	0	0	0	1	0
0	1	0	1	0	0	1
1	0	0	0	1	1	0
1	1	1	1	0	1	0
Gate Symbol						
Functional Notation		\wedge	\vee	\oplus	\uparrow	\downarrow

Part A

2. AND Truth table

A	B	AND
0	0	0
1	1	1
Functional notation		\wedge

